

Theoretical Values

* DC Voltage

$$V_{DC} \approx V_{peak} - 2V_D$$

$$V_{peak} = 28.3V; V_D = 0.7V$$

$$V_{DC} \approx 28.3 - 1.4 = \boxed{26.9V}$$

* Load Current

$$I_{Load} = \frac{V_{DC}}{R_L}$$

$$V_{DC} = 26.9; R_L = 510\Omega$$

$$I_{Load} = \frac{26.9}{510} = \boxed{0.0530 \approx 53mA}$$

* Ripple Voltage

$$\Delta V_r = \frac{I_{Load}}{f_r \times C}$$

$$I_{Load} = 52mA; f_r = 120Hz; C = 470\mu F$$

$$\Delta V_r = \frac{0.0530}{120 \times 470 \times 10^{-6}} = \boxed{0.922V_{PP}}$$